

# EE2703 Week 7

Anand Uday Gokhale Roll Number : EE17B158

March 2019

## 1 Introduction

This week's assignment involves the analysis of filters using laplace transforms. Python's symbolic solving library, sympy is a tool we use in the process to handle our requirements in solving Modified Nodal Analysis equations. Besides this the library also includes useful classes to handle the simulation and response to inputs.

Coupled with scipy's signal module, we are able to analyse both High pass and low pass filters, both second order, realised using a single op amp

### 1.1 Low pass Filter

The low pass filter we use gives the following matrix after simplification of Modified Nodal Equations.

$$\begin{bmatrix} 0 & 0 & 1 & -1/G \\ \frac{-1}{sR_2C_2} & 1 & 0 & 0 \\ 0 & -G & G & 1 \\ \frac{-1}{R_1} - \frac{1}{R_2} - s * C_1 & \frac{1}{R_2} & 0 & sC_1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_p \\ V_m \\ V_o \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ \frac{-V_i(s)}{R_1} \end{bmatrix}$$

---

```
def lowpass(R1,R2,C1,C2,G,Vi):
    s= sympy.symbols("s")
    A = sympy.Matrix([[0,0,1,-1/G],\
                      [-1/(1+s*R2*C2),1,0,0],\
                      [0,-G,G,1],\
                      [-1/R1-1/R2-s*C1,1/R2,0,s*C1]])
    b= sympy.Matrix([0,0,0,-Vi/R1])
    V = A.inv()*b
    return A,b,V
```

---

The magnitude bode plot for the filter looks like:

 


Figure 1: Lowpass filter magnitude response

## 1.2 High pass Filter

The high pass filter we use gives the following matrix after simplification of Modified Nodal Equations.

$$\begin{bmatrix} 0 & -1 & 0 & 1/G \\ \frac{s*C_2*R_3}{1+s*C_2*R_3} & 0 & -1 & 0 \\ 0 & G & -G & 1 \\ -s*C_2 - \frac{1}{R_1} - s*C_1 & 0 & s*C_2 & \frac{1}{R_1} \end{bmatrix} \begin{bmatrix} V_1 \\ V_p \\ V_m \\ V_o \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ -V_i(s) * s * C_1 \end{bmatrix}$$

---

```
def highpass(R1,R3,C1,C2,G,Vi):
    s= sympy.symbols("s")
    A=sympy.Matrix([[0,-1,0,1/G],
        [s*C2*R3/(s*C2*R3+1),0,-1,0],
        [0,G,-G,1],
        [-s*C2-1/R1-s*C1,0,s*C2,1/R1]])
    b=sympy.Matrix([0,0,0,-Vi*s*C1])
    V=A.inv()*b
    return (A,b,V)
```

---

The magnitude bode plot for the filter looks like:

 


Figure 2: High pass filter magnitude response

## 2 Assignment Questions

### 2.1 Question 1

The unit step response for the low pass filter:

---

```
def symToTransferFn(Y):
    Y = sympy.expand(sympy.simplify(Y))
    n,d = sympy.fraction(Y)
    n,d = sympy.Poly(n,s), sympy.Poly(d,s)
    num,den = n.all_coeffs(), d.all_coeffs()
    num,den = [float(f) for f in num], [float(f) for f in den]
    return num,den

def stepresponse(Y):
    num,den = symToTransferFn(Y)
    den.append(0)
    H = sp.lti(num,den)
    t,y=sp.impulse(H,T = np.linspace(0,1e-3,10000))
    plt.plot(t,y)
    plt.show()
    return

s = sympy.symbols("s")
A,b,V=lowpass(10000,10000,1e-9,1e-9,1.586,1)
stepresponse(V[3])
```

---

 


Figure 3: System Response with Decay = 0.5

## 2.2 Question 2

We now see what happens with a input as a sum of sinusoids.

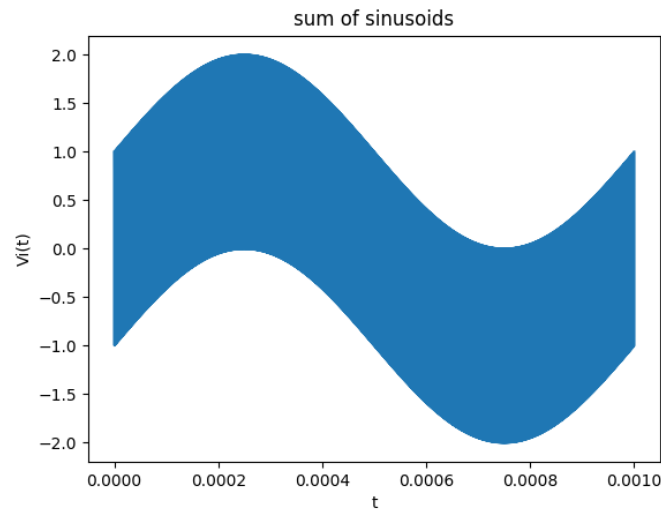


Figure 4: Sum of sinusoids

---

```
def inputs(t):  
    return (np.sin(2000*np.pi*t)+np.cos(2e6*np.pi*t))  
  
def inp_reponse(Y,inp=inputs,tlim=1e-3):  
    num,den = symToTransferFn(Y)  
    H = sp.lti(num,den)  
    t = np.linspace(0,tlim,100000)  
    t,y,svec = sp.lsim(H,inp(t),t)  
    plt.plot(t,y)  
    plt.show()  
    return
```

---

We notice that the high frequency part has been attenuated.

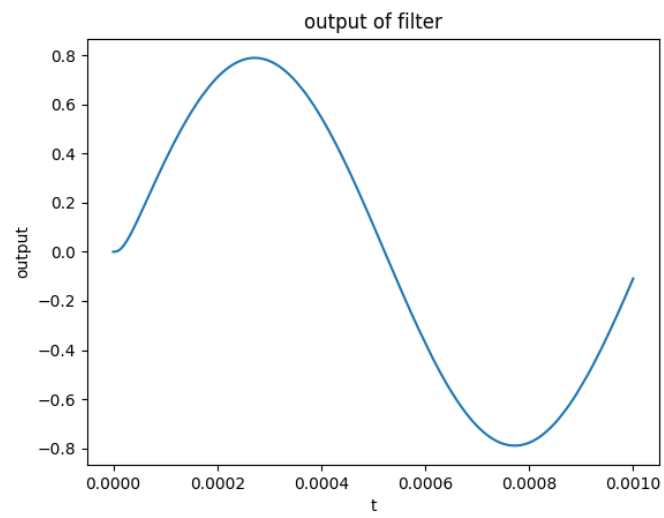


Figure 5: Output of low pass filter

### 2.3 Question 3

See section 1.2 for magnitude plot

The High pass filter attenuates high frequencies, leaving behind the higher frequency component in the sum of sinusoids.

 


Figure 6: Output of high pass filter for sum of sinusoids

### 2.4 Question 4

#### 2.4.1 High frequency damped sinusoid

The High frequency damping sinusoid is given by:

$$f(t) = \cos(10^7 t) * e^{-3000t} \quad (1)$$

It is expected that it will be fully attenuated by the Low pass filter while it will pass through the high pass filter with almost no change.

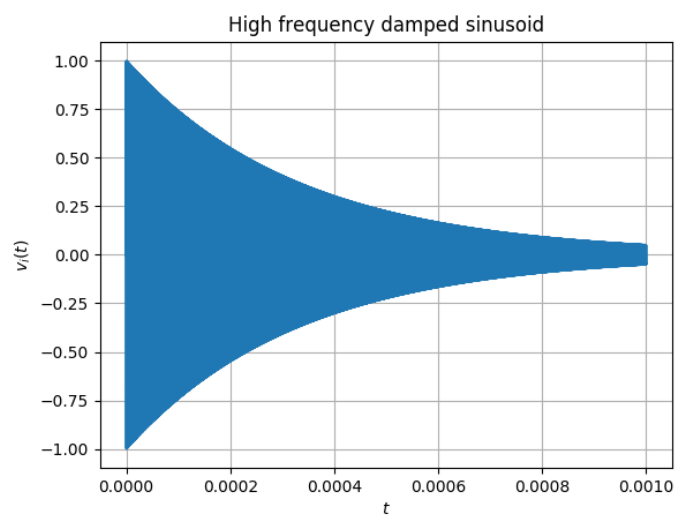


Figure 7: High frequency damped sinusoid

 


Figure 8: Damped Sinusoid response from Low pass filter



 


Figure 9: Damped Sinusoid response from High pass filter

### 2.4.2 Low frequency damped sinusoid

The High frequency damping sinusoid is given by:

$$f(t) = \cos(10^3 t) * e^{-1000t} \quad (2)$$

It is expected that it will be fully attenuated by the Low pass filter while it will pass through the high pass filter with almost no change.

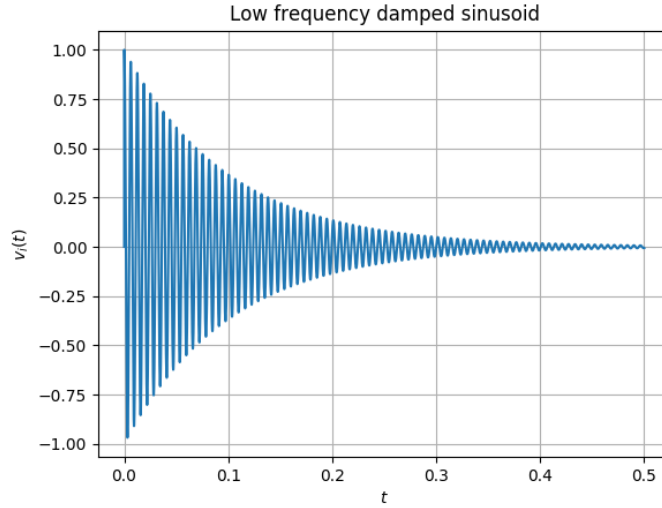


Figure 10: Low frequency damped sinusoid

The low pass filter responds by letting the low frequency sinusoid pass through without much additional attenuation. The output decays as the input also decays. The high pass filter responds by quickly attenuating the input. Notice that the time scales show that the high pass filter response is orders of magnitudes faster than the low pass response. This is because the input frequency is below the cutoff frequency, so the output goes to 0 very fast.

## 2.5 Question 5

The unit step response, as expected is high at  $t=0$  when there is an abrupt change in the input. Since there is no other change at large time values outside the neighbourhood of 0, the Fourier transform of the unit step has high values near 0 frequency, which the high pass filter attenuates.

## 3 Conclusion

In conclusion, the sympy module has allowed us to analyse quite complicated circuits by analytically solving their node equations. We then interpreted the

 


Figure 11: Damped Sinusoid response from Low pass filter

 


Figure 12: Damped Sinusoid response from High pass filter

solutions by plotting time domain responses using the signals toolbox. Thus, sympy combined with the scipy.signal module is a very useful toolbox for analyzing complicated systems like the active filters in this assignment.

 


Figure 13: Step response of high pass filter